

Feivel Jethro Ezekieli

21/402312/PA/21042



I. Direction of Stepper motor

Clock Wise

II. Direction of Stepper Motor using IC ULN2003

Clockwise

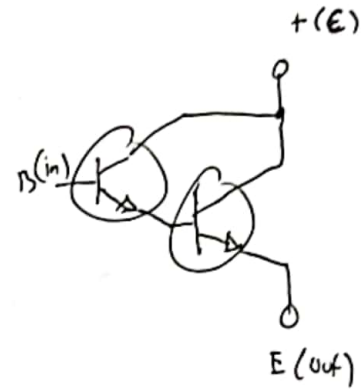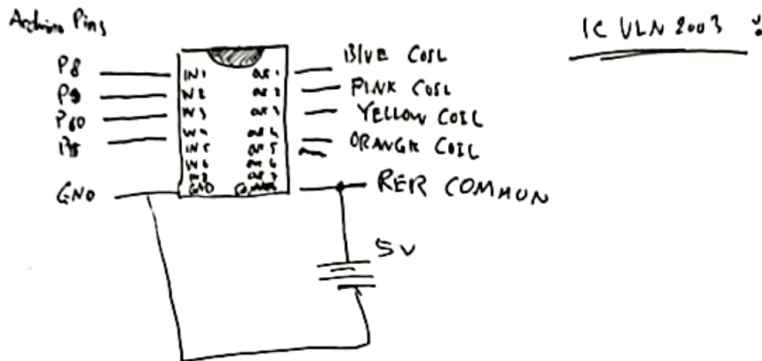III. Use 2nd Circuit make a delay variation and note it using step watch



Darlington pair transistor

DELAY	RPM
40	0,5
35	0,55
30	0,98
25	1,15
20	1,42
15	2
10	3
5	6
3	10
1	0

[Signature]